



Efficient Charging of Supercapacitors with Energy Harvesters

Pierre Mars

Darnell Power Forum, September 19-21, 2012


- Wireless sensors coupled with low power energy harvesters are becoming ubiquitous
- An high power energy store is required to provide peak power for data collection and transmission
- Supercapacitors are an ideal energy storage device for this function
- What supercapacitor properties are important for this function?
- What is the optimum solution to charge the supercapacitor?

- Why use a supercapacitor?
- Supercapacitor properties
(What you need to know when designing your system)
 - Temperature performance
 - Leakage current
 - Charge current
 - Cell balancing
- Interfacing the supercapacitor to your energy source
 - Supercapacitors just want current, not constant voltage
 - If the energy harvester delivers short cct current, is it better to charge directly, or use a Peak Power Tracking charger IC?


- Physical charge storage
 - “Infinite” cycle life
- Low impedance (ESR)
 - High power delivery
 - Transmission over a cellular network
- Super High C
 - Energy to deliver the power for the duration needed
- High power delivery at low temps (-40°C)
- Easy to charge
 - Just need a charge current and over-voltage protection
- Low leakage current
- Available in thin, small form-factors




Normalised ESR vs Temp

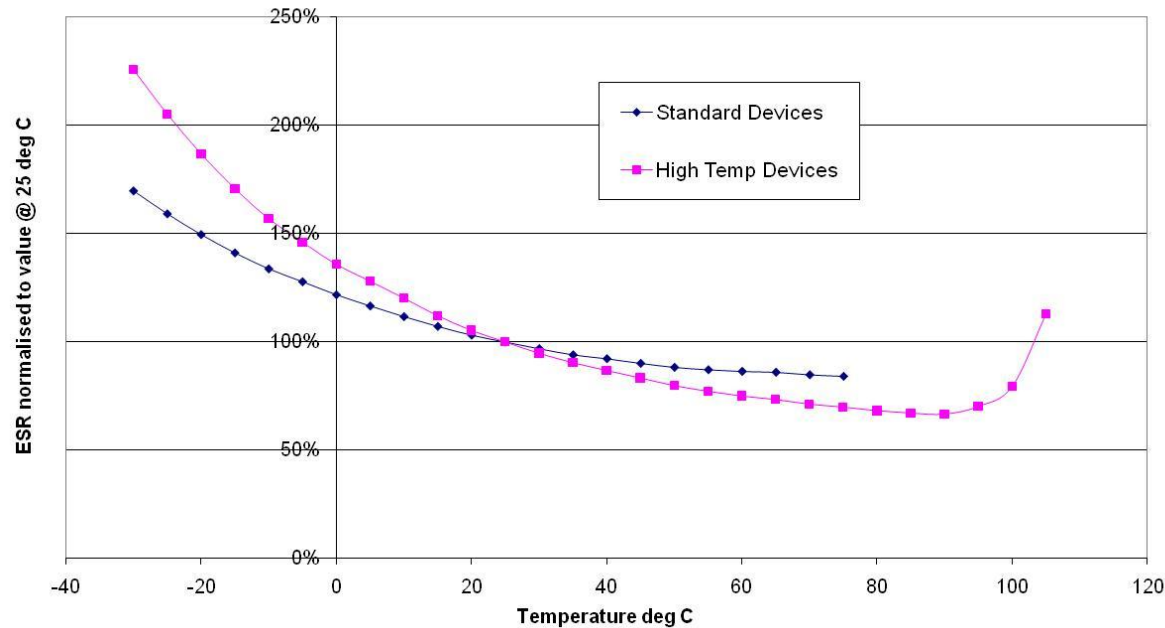


Normalised C vs Temp

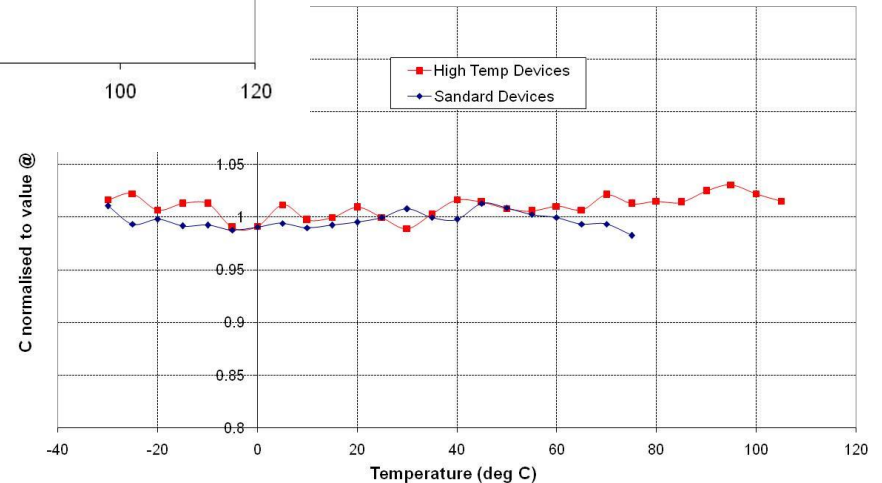


Leakage Current

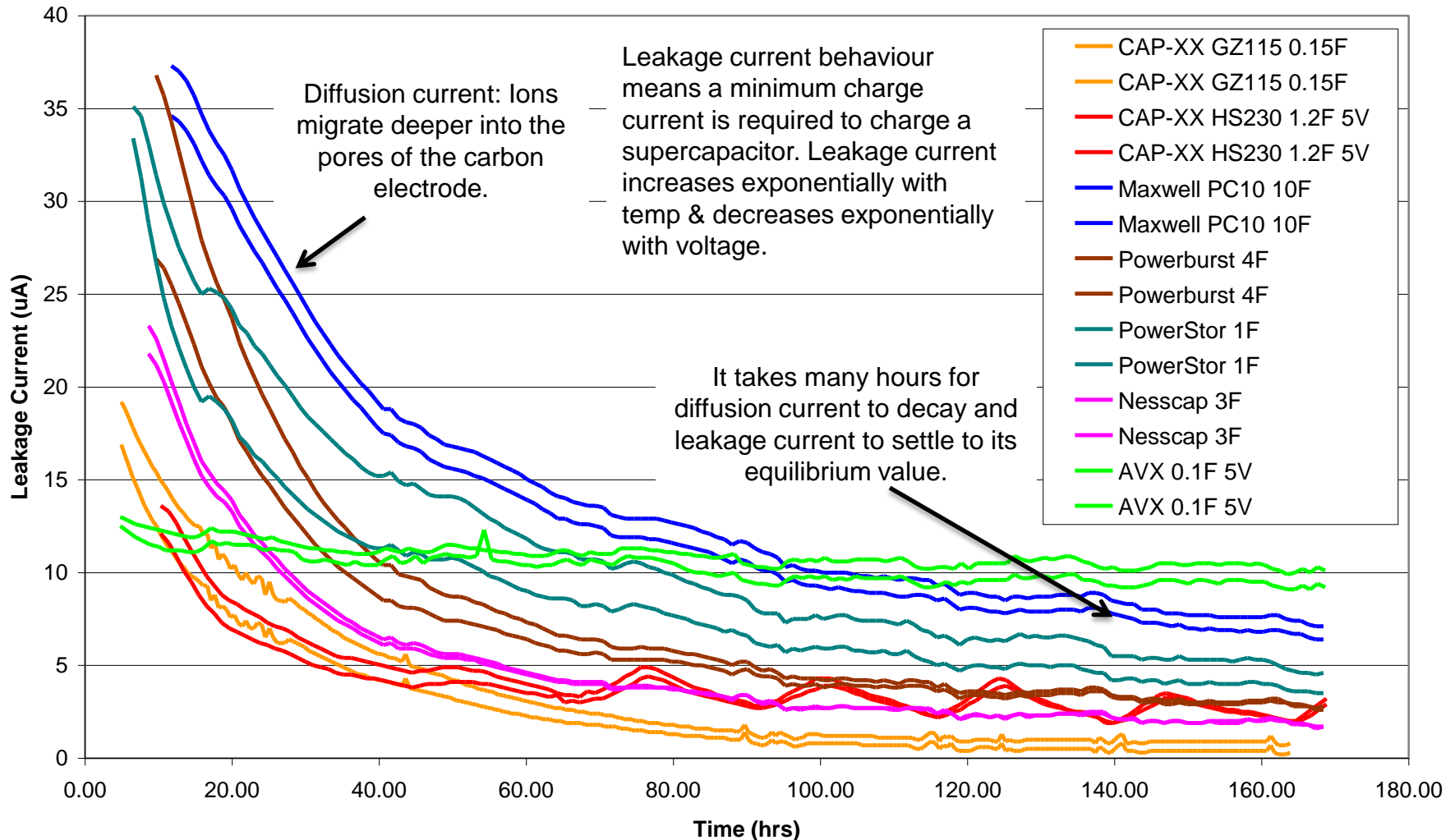


Charging at 20uA

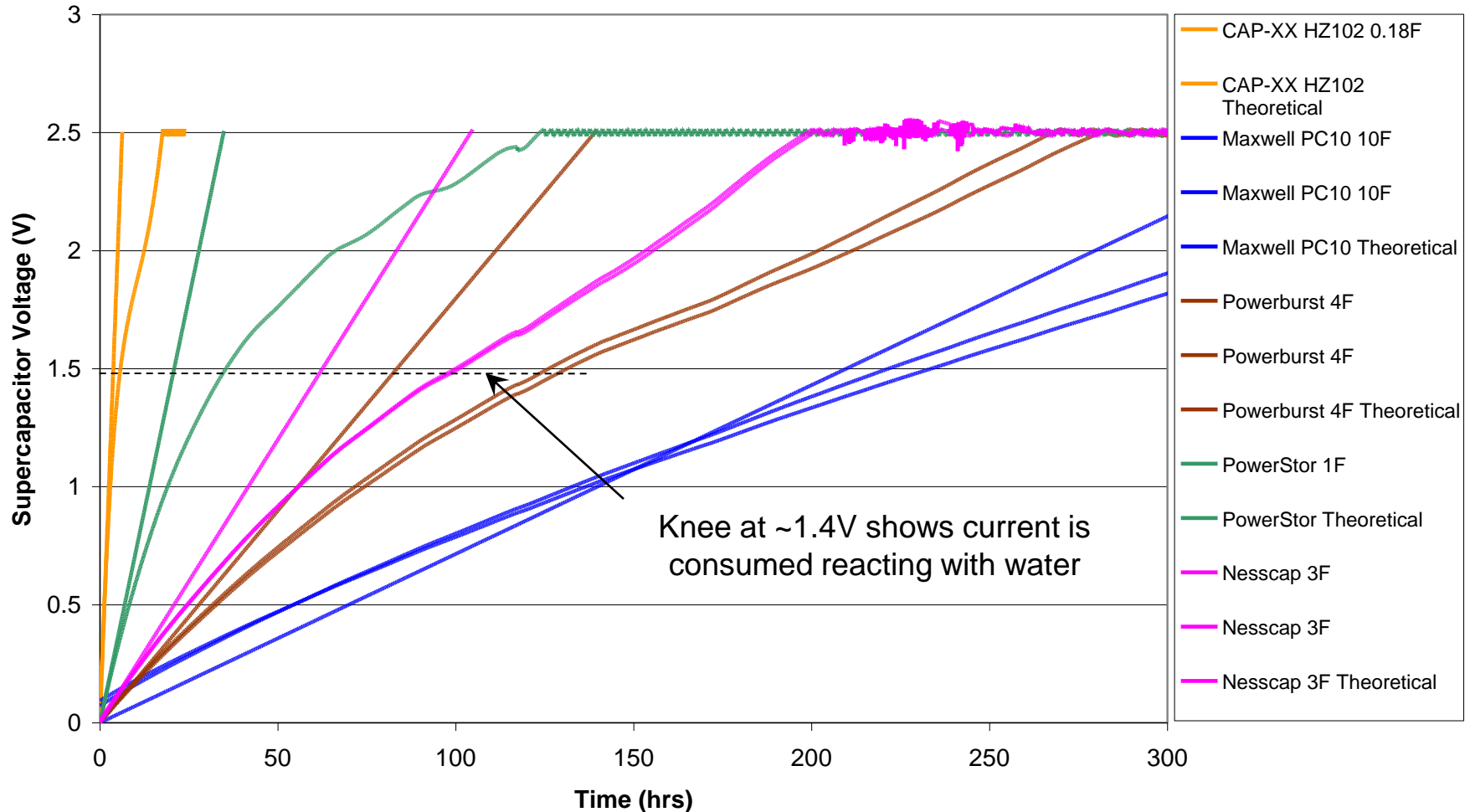


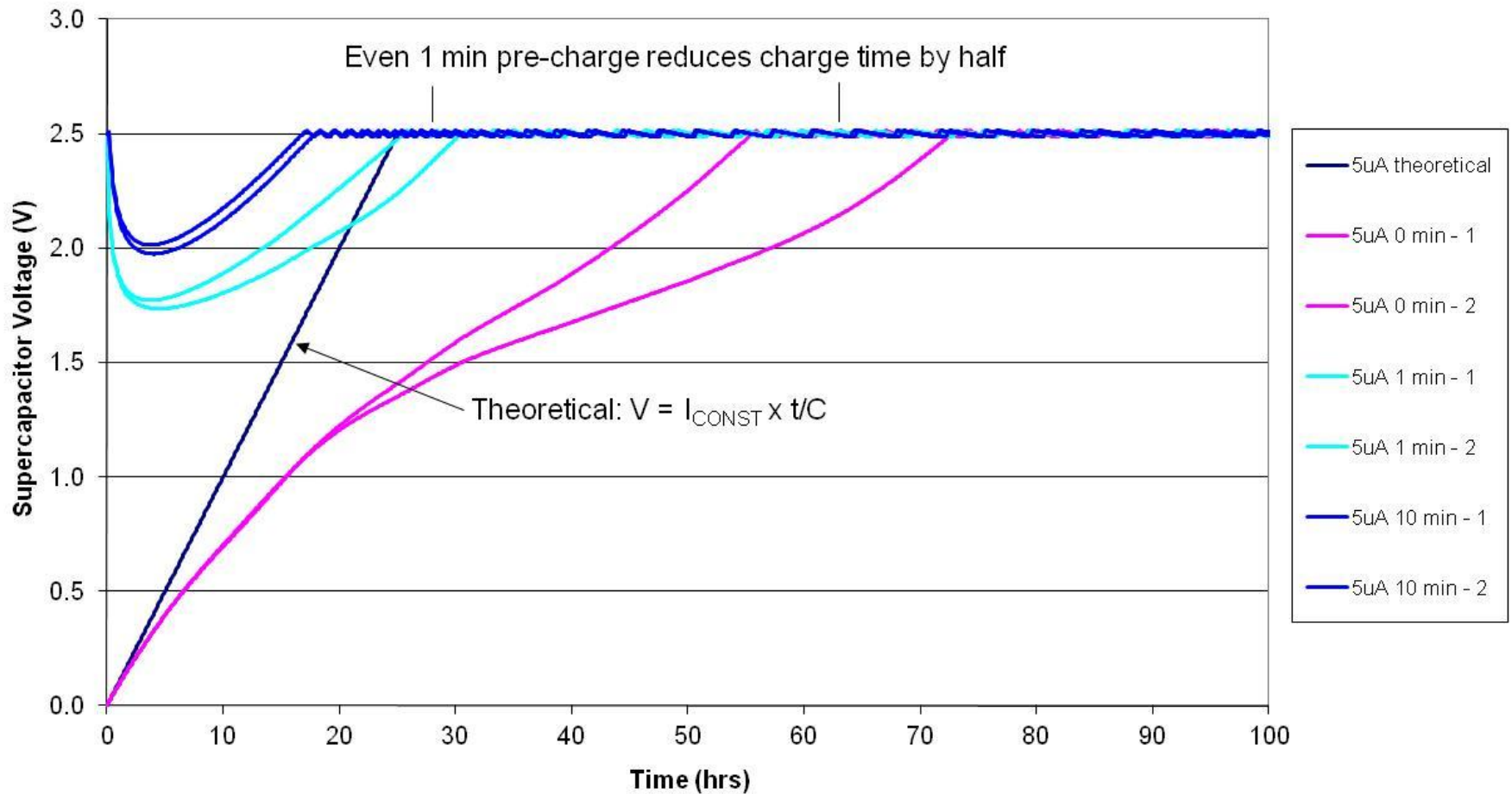HZ102 charging to 2.5V at 5uA after varying time at pre-charge at 2.5V, 10mA




Leakage Current

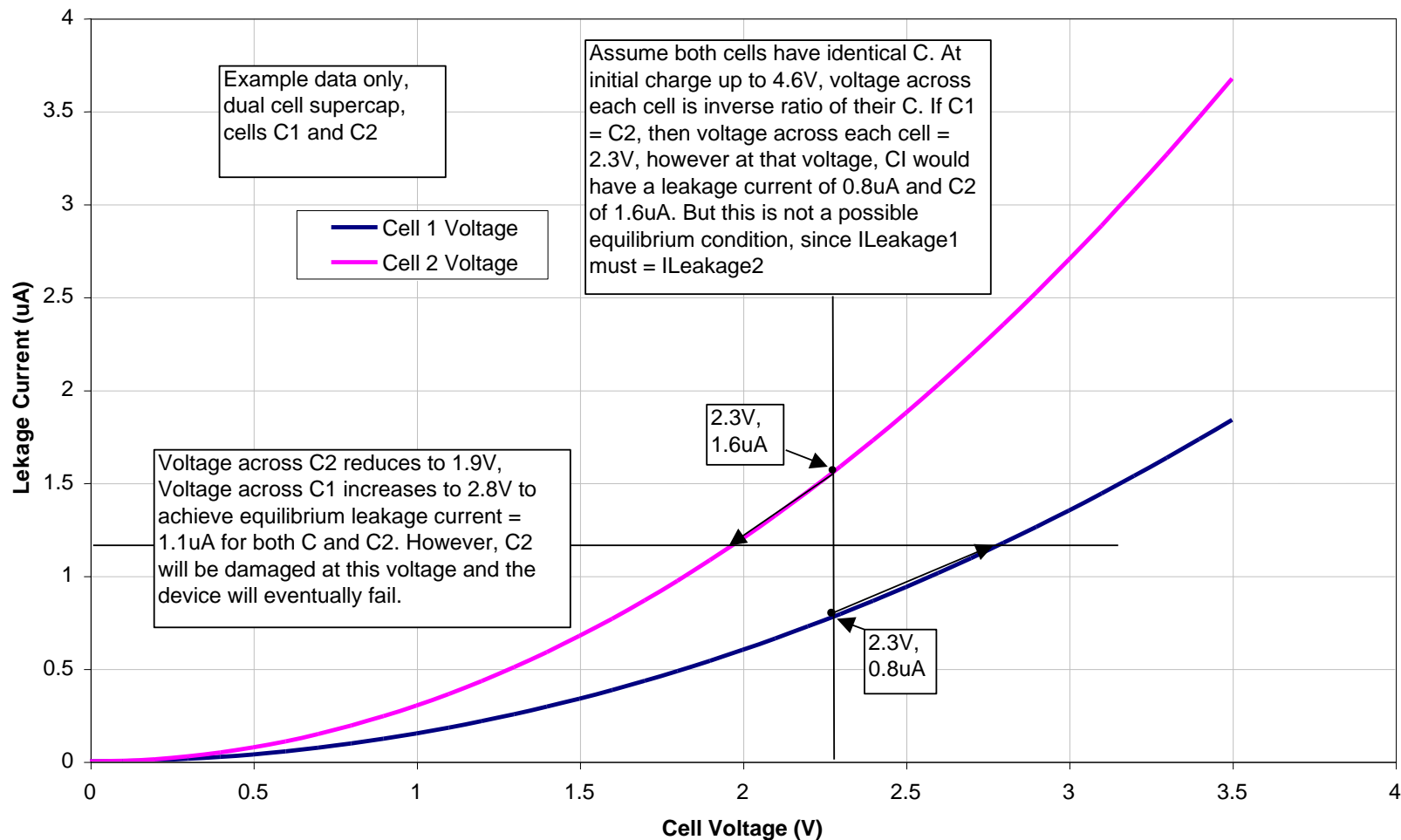


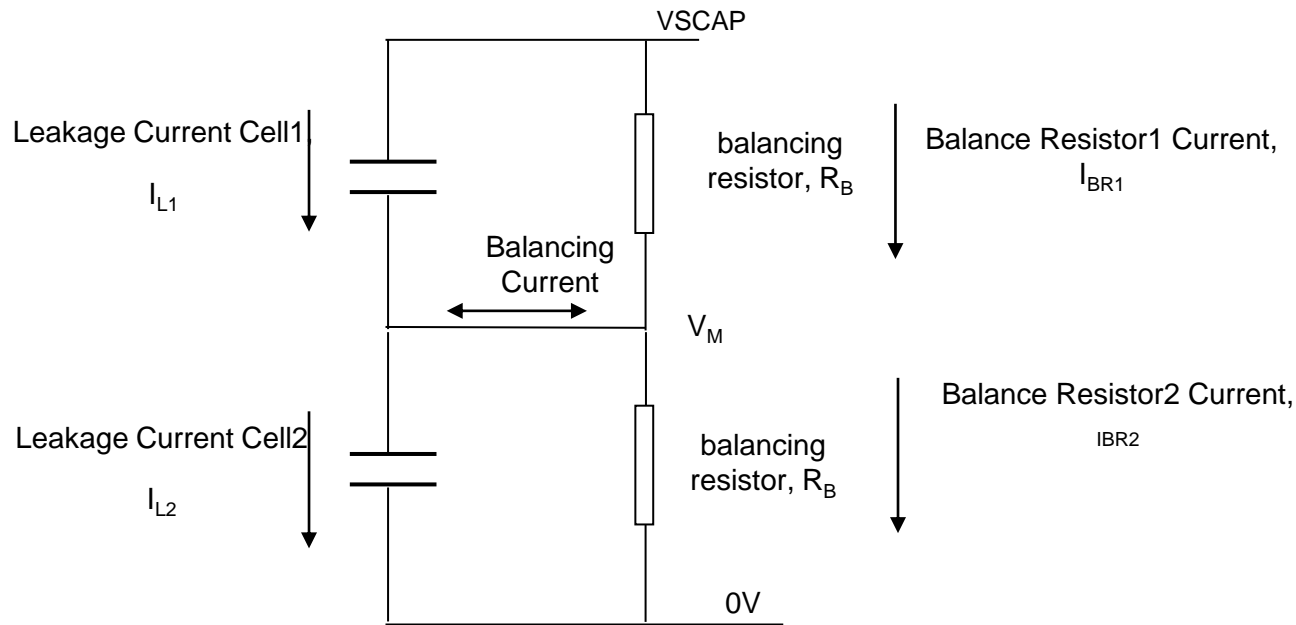

- The purpose of this circuit is to maintain V_M close to $V_{SCAP} / 2$
- $V_M = R_B \times I_{BR2} = R_B \times (I_{BR1} - \text{Balancing Current})$
- For this circuit to work, Balancing Current must be $\ll I_{BR1}, I_{BR2}$
- V_M must be prevented from going $\gg V_{SCAP} / 2$ or $\ll V_{SCAP} / 2$ for any significant length of time
- SIMPLE but HIGH CURRENT SOLUTION ($\sim 100\mu A$ through the resistors)

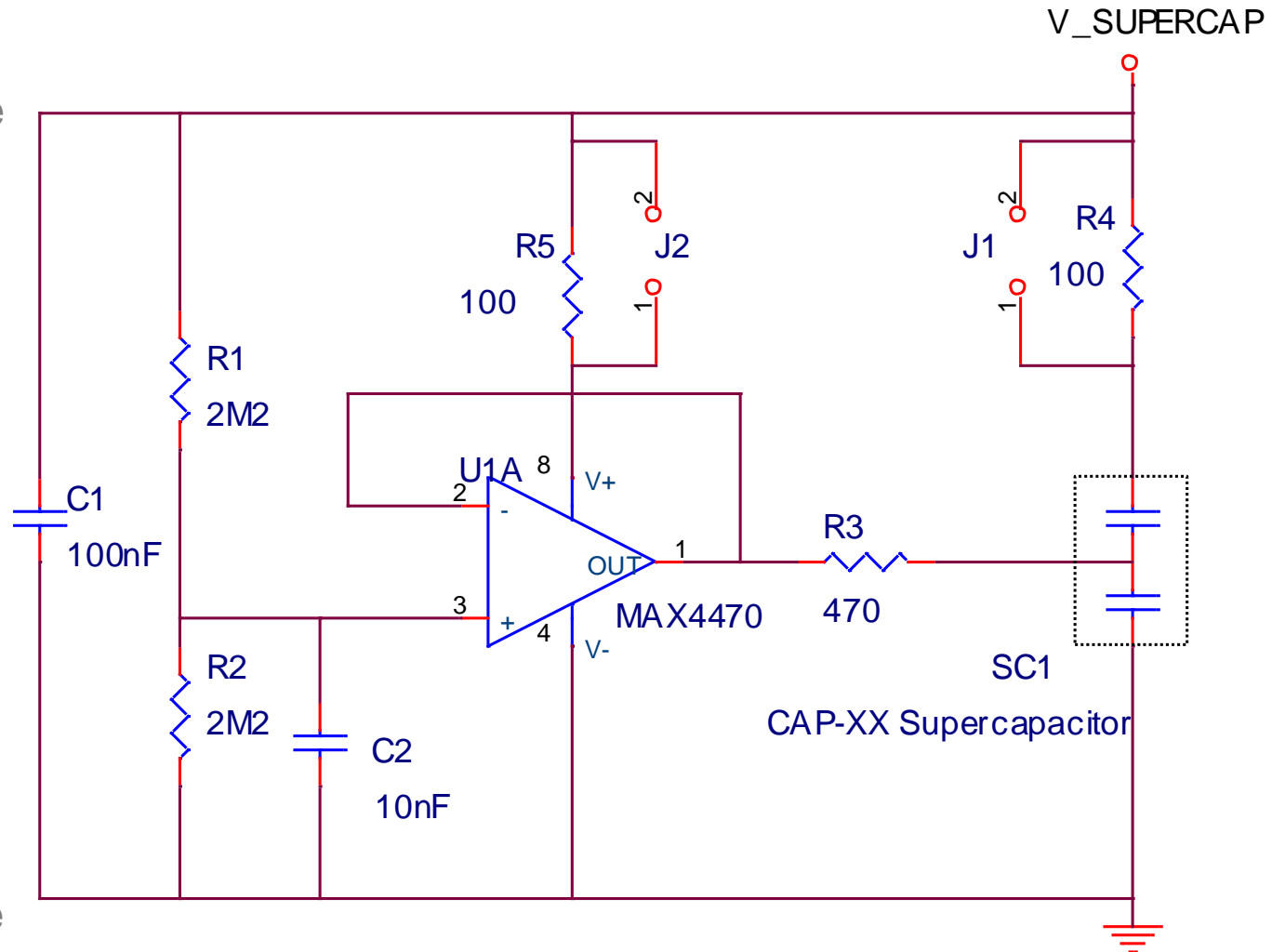- 2 capacitor cells in series need voltage balancing, or slight differences in leakage current may result in one cell going over-voltage
- Low current rail-rail op amp, $< 1\mu\text{A}$
- Can source or sink current, 11mA
- Supplies or sinks the difference in leakage current between the 2 cells to maintain balance



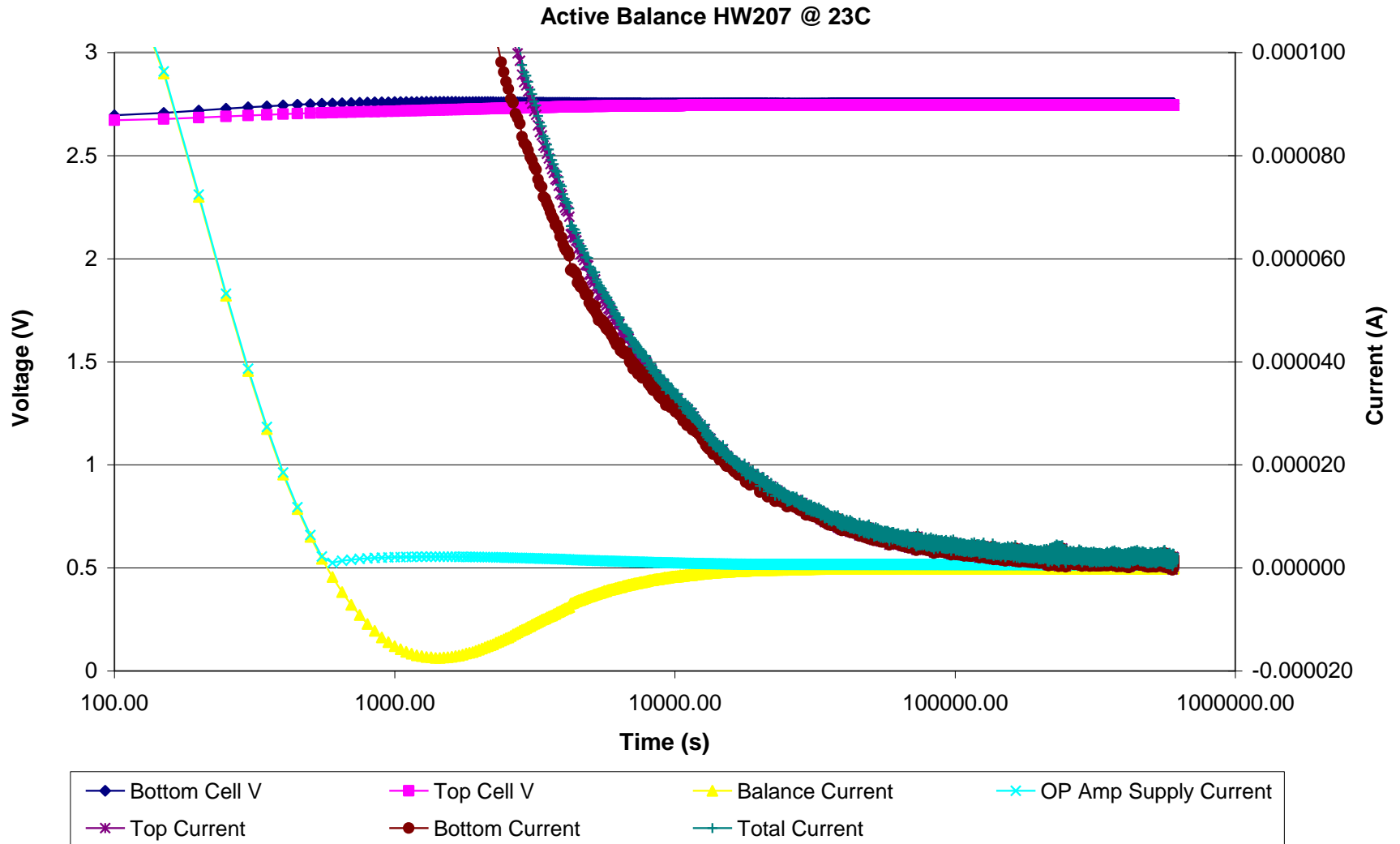


Supercapacitor Interface Circuits

Design principles:

1. Must behave gracefully into a short circuit
2. Must start charging from 0V
3. Must provide over-voltage protection
4. Must prevent the supercapacitor from discharging into the source
5. Should be designed for maximum efficiency


- A discharged supercapacitor will look like a short circuit to your energy source
- Most energy harvesters don't care – will deliver current into a short circuit
- Definitely a problem for batteries, and some other power supplies
 - Interface electronics must manage this either in the design:
 - Keep the source near its maximum power point
 - Graceful behaviour into a short circuit
 - Or with a separate current limit
 - AAT4610 (www.cap-xx.com/resources/app_notes/an1002.pdf)
 - Or with a supercapacitor charging IC
 - LTC3225

Example 1: Solar cells

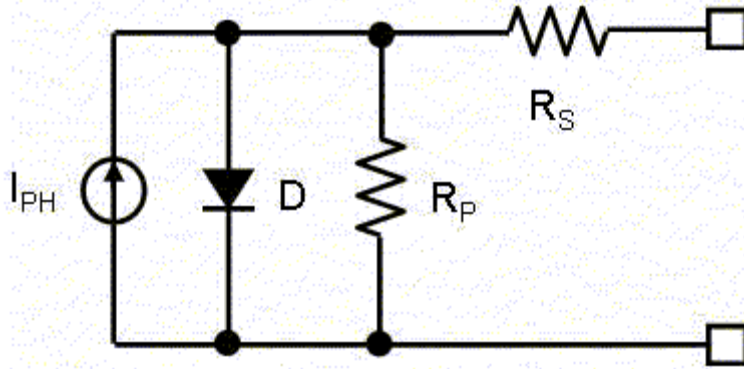


Simplified Circuit Model of a Solar Cell

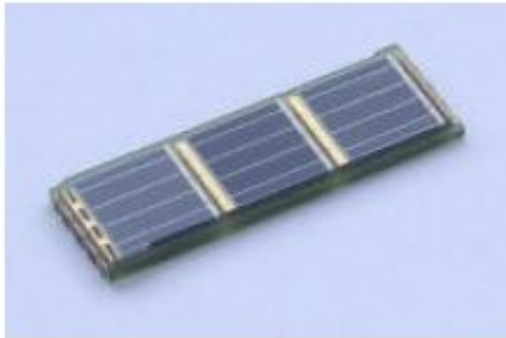XOB17, 22mm x 7mm x 1.6mm
used for measurements in
following slides




- I_{PH} generates current \propto light falling on the cell
- If no load connected all the current flows through the diode whose forward voltage = V_{OC} .
- R_P represents leakage current
- R_S represents connection losses, usually not significant
- Will deliver current into a short circuit (discharged supercapacitor)
- Will discharge the load if light level drops

Cell Current/Voltage Behavior

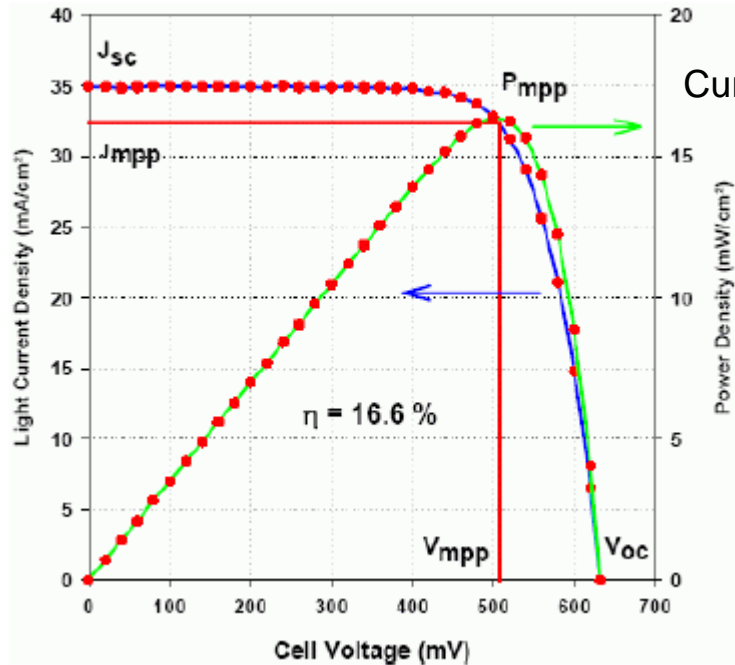


Curves provided in data sheet

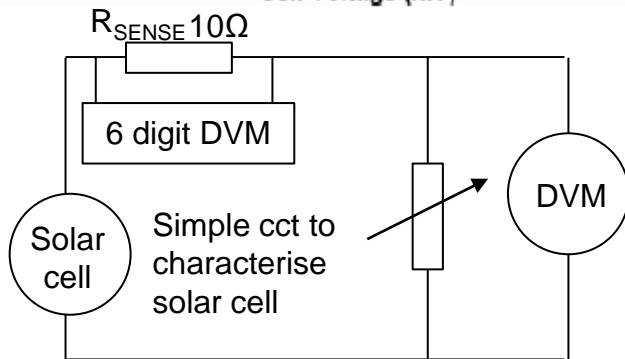Curves developed in lab in our light conditions



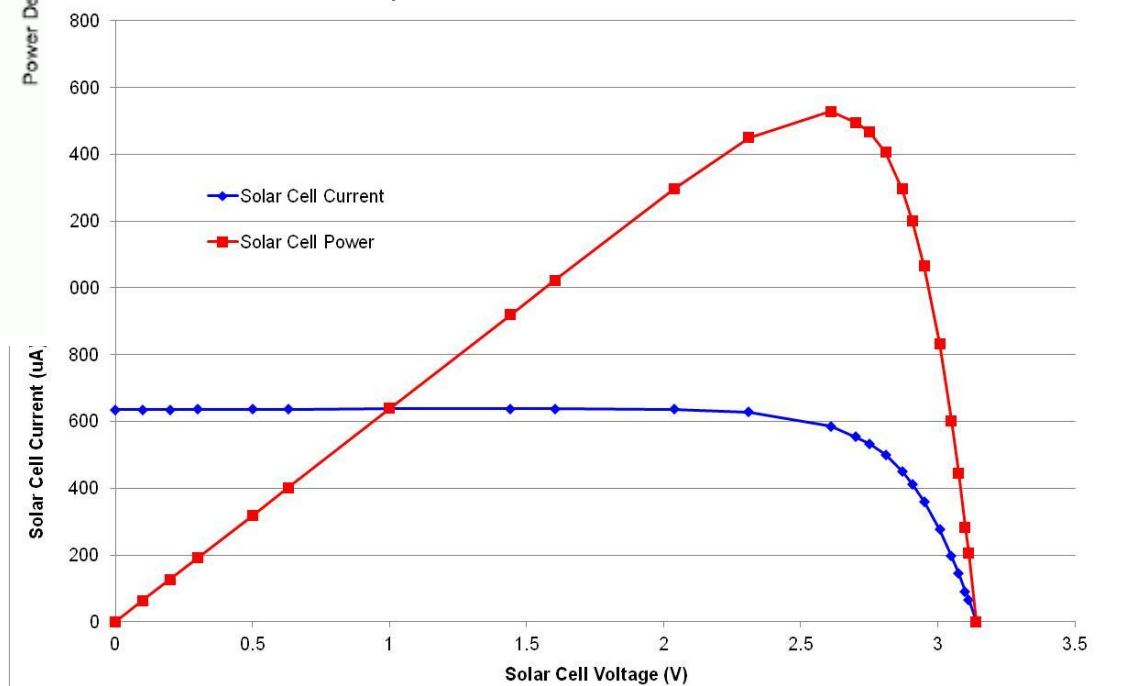
Solar Array Characterisation, 2 x XOB17-04x3 in series




- $V_{IN} \cdot I_{IN} = V_{OUT} \cdot I_{OUT} \times \eta$
- If $\eta = 90\%$, $I_{OUT} = P_{IN} \times 90\% / V_{OUT}$
- PPT maximises P_{IN} , hence I_{OUT}
- Gives very high charge current when V_{OUT} is low (start of supercap charging), $> I_{SCAP}$ of energy harvester

Other considerations for PPT IC:

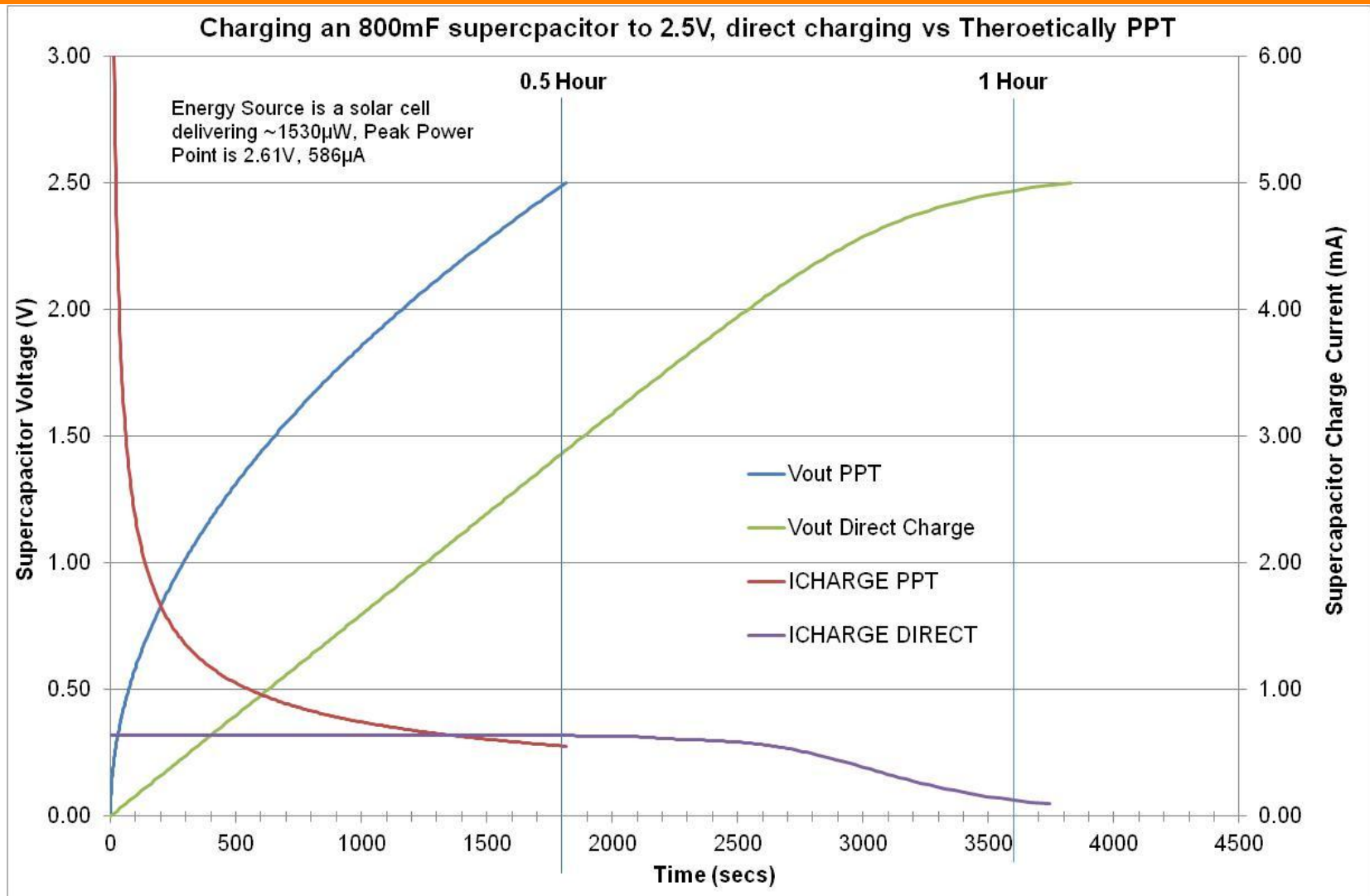
- Need $P_{SUPPLY} \ll P_{IN}$
- Must behave well into a short cct (some ICs are designed to charge a battery, and do not understand 0V on their o/p, or cannot have user-programmable o/p voltage)



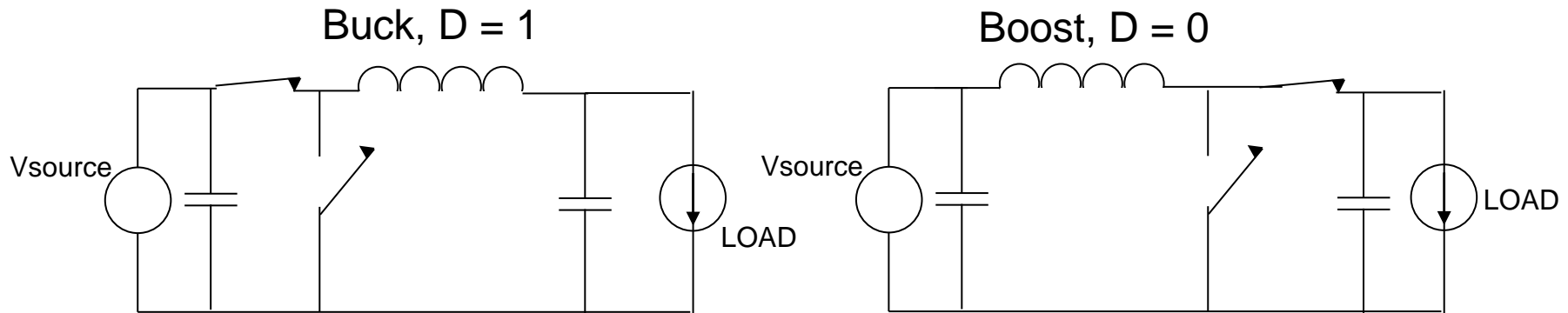- DC:DC doesn't operate that way when $V_{OUT} \ll V_{TARGET}$




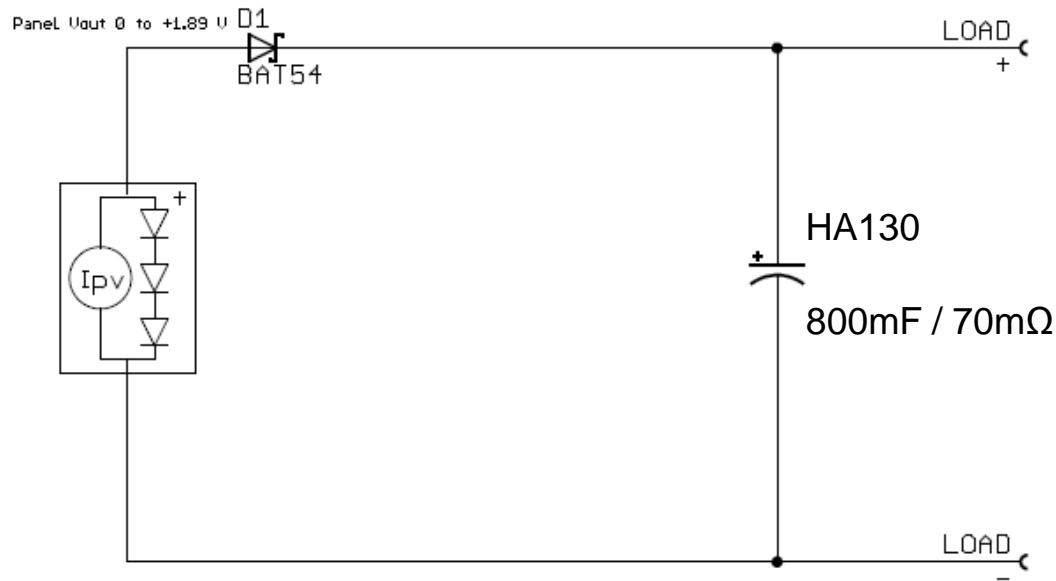
- Unlike a battery, this is the case when charging a supercapacitor from 0V
- Looks like direct charging
- Need a DC:DC where V_{TARGET} is just above V_{OUT} until V_{OUT} approaches the final value of V_{TARGET}



- Simplest circuit, starts charging from 0V
- $V_{OC} < 2.7V$ at maximum light level
- D1 prevents the supercapacitor from discharging back into the solar cell when light levels fall
- BAT54 chosen for D1 due to low V_F . V_F is $< 0.1V$ at currents $< 10\mu A$
- HA130 provides excellent energy storage & power delivery
- **Fastest charge. But will NOT charge if $V_{SOLAR} < V_{SCAP}$** (e.g. if light level falls)

HA130 Direct Charge

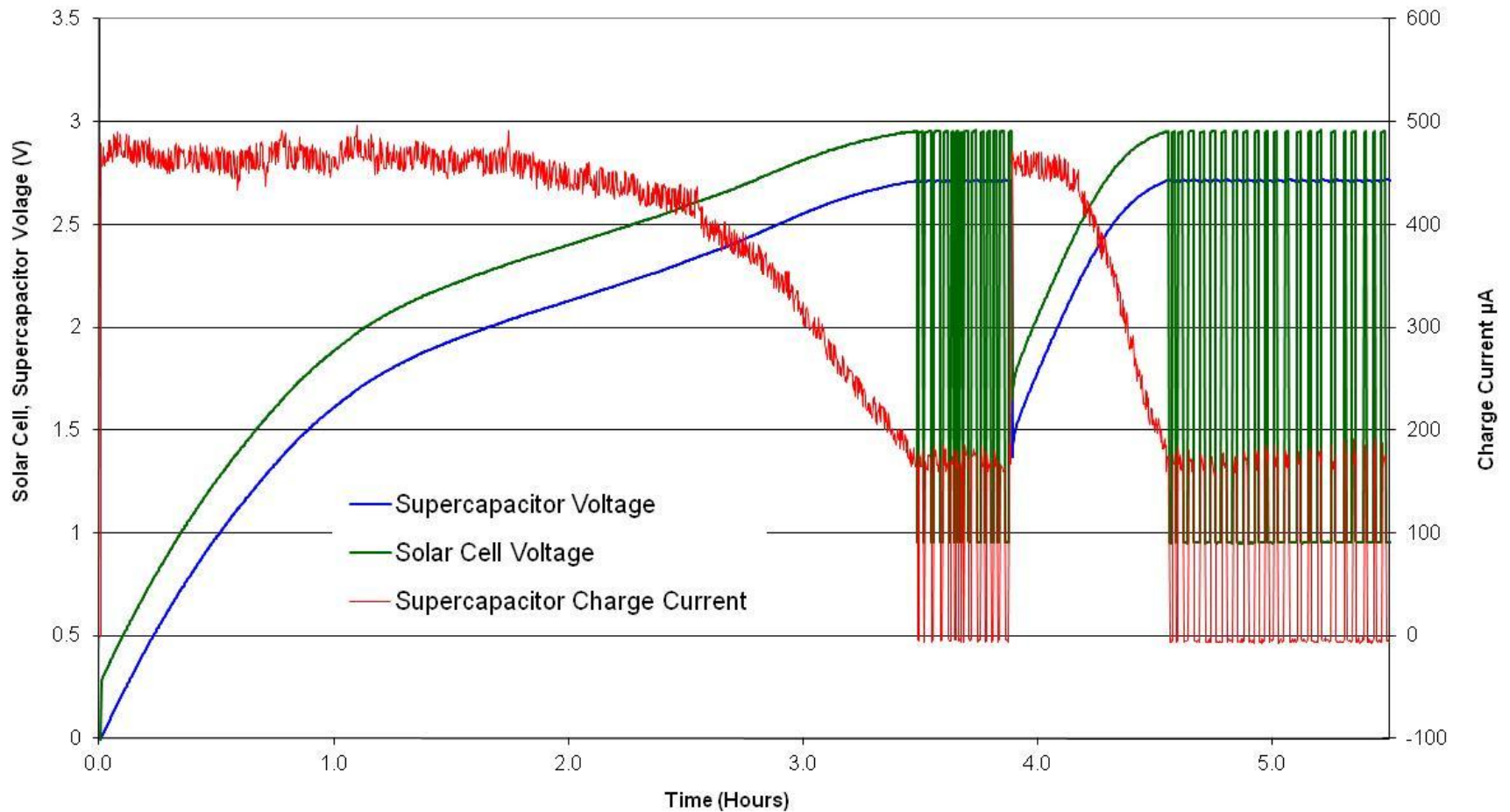


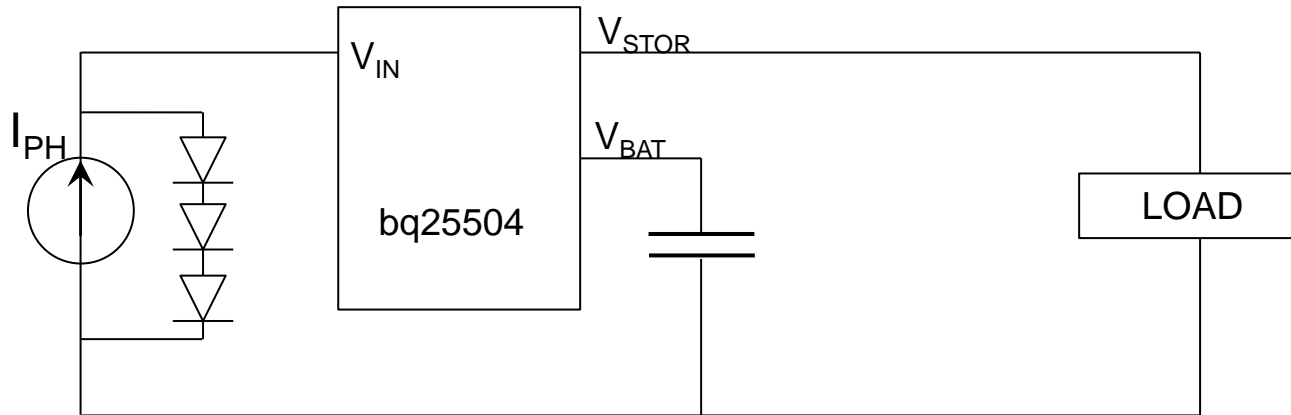


- Charge using bq25504 boost converter with Peak Power Tracking (PPT)
- The bq25504 has very inefficient “cold start” charging if $V_{BAT} < \sim 1.5V$
- It take ~ 67 hrs for the bq25504 to charge an HA130 from 0V to 1.5V with a solar cell delivering $350\mu W$ peak power (“cold start”)
- It takes another hour to reach 2.7V with the boost converter running normally with PPT
- **Slowest charge. But WILL charge if $V_{SOLAR} < V_{SCAP}$ and $V_{SCAP} > 1.5V$** (e.g. if light level falls with the supercapacitor partially or fully charged)




Charge with bq25504 Waveforms

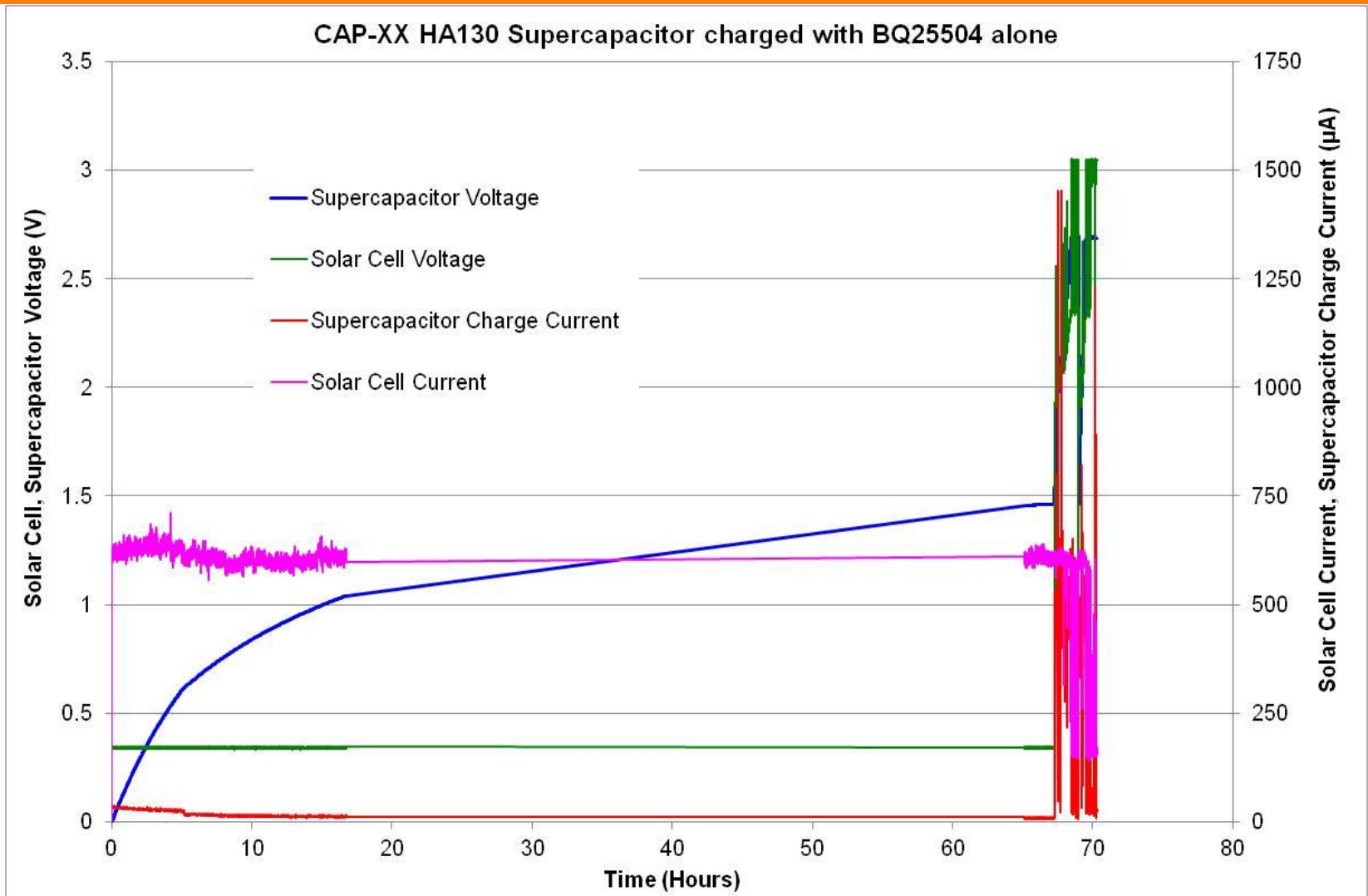

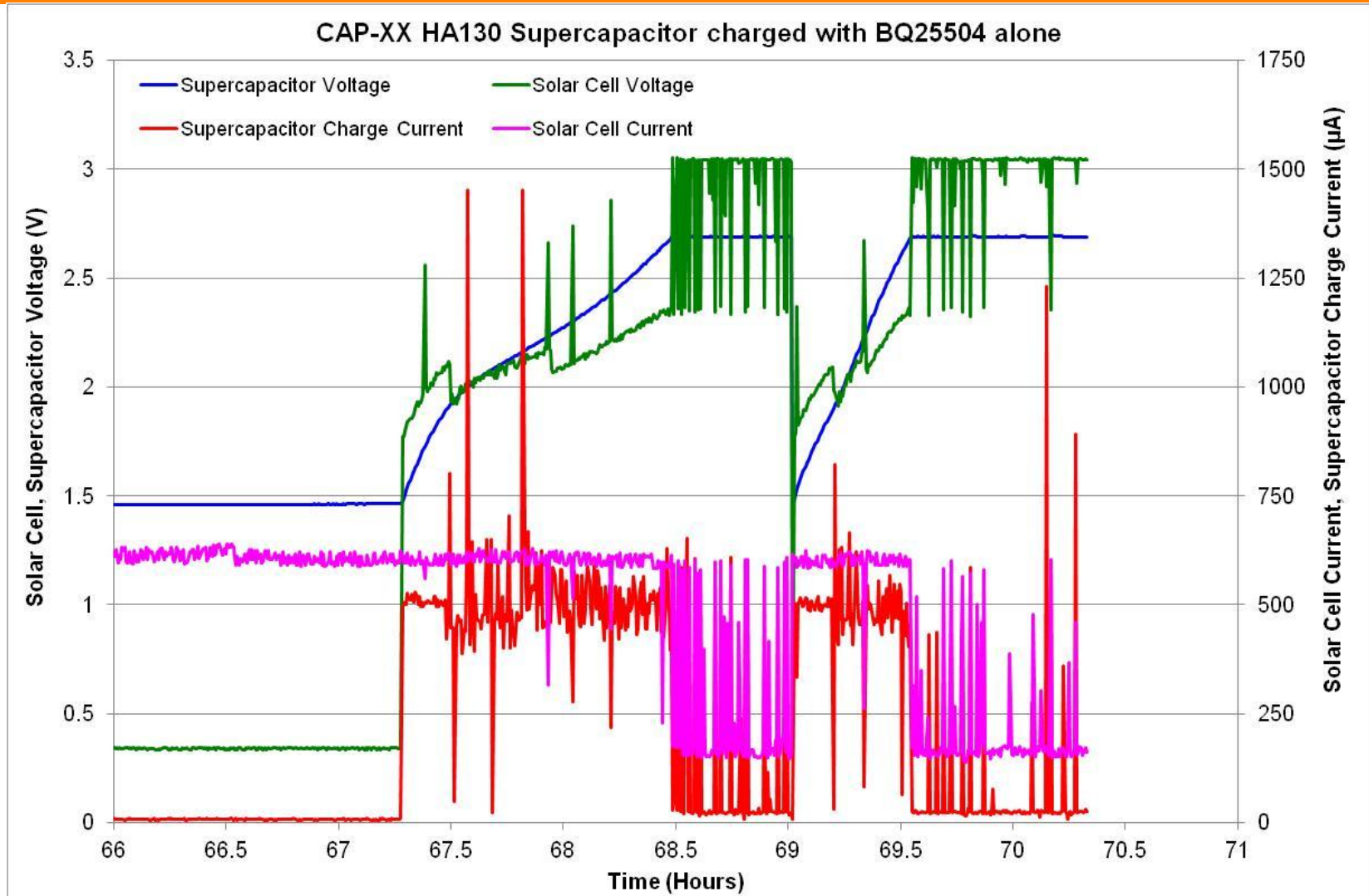

- The bq25504 has very inefficient “cold start” charging if $V_{BAT} < \sim 1.5V$
- Charging an HA130 from 0V with a solar cell with 350μW peak power takes ~67hrs to reach 1.5V
- At this point, the bq25504 switches from “cold start” mode to normal operation with PPT, and takes only 1 hour to reach 2.7V
- **Conclusion:** The bq25504 does not behave well into a short cct, since it invokes battery protection features

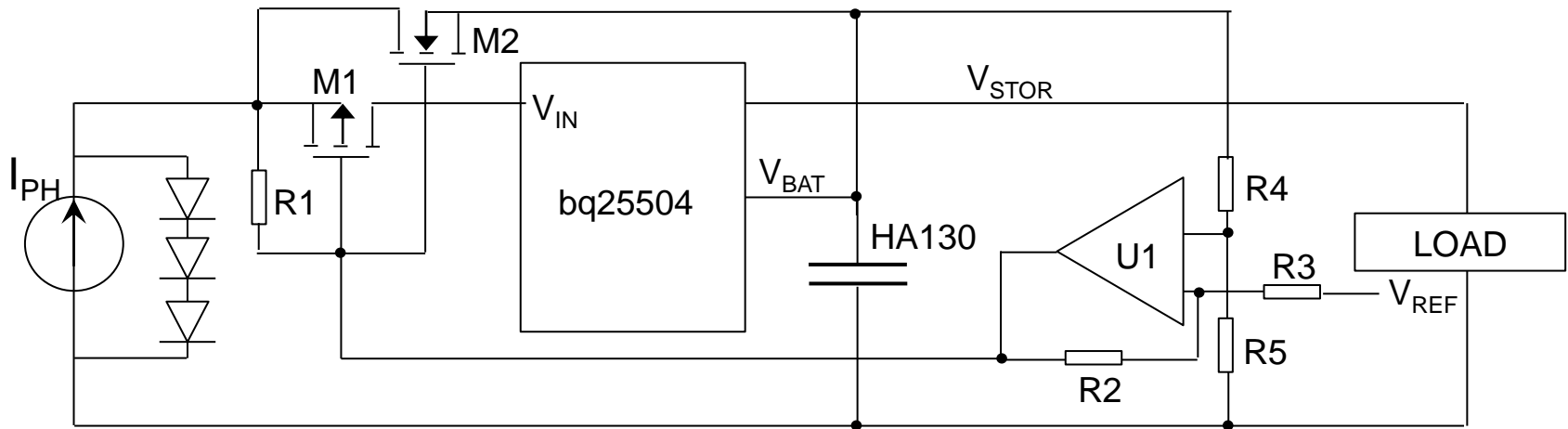


- Supercap charges directly from 0V using NFET M2 to bypass bq25504. M1 is OFF, stopping the bq25504 from pulling down the solar cell voltage
- When the supercap reaches ~1.8V, the comparator turns M1 ON, connecting the bq25504 to the solar cell, and turns M2 OFF, preventing the solar cell over-charging the supercap if $V_{\text{SOLAR_OC}} > V_{\text{SCAP_MAX}}$
- The supercapacitor target voltage is now set by the bq25504. **There is no possibility of the supercapacitor being over-voltage**
- Achieve fast initial charge + fast charge with PPT once $V_{\text{SCAP}} > 1.8\text{V}$
- **Fast charge, and WILL charge if $V_{\text{SOLAR}} < V_{\text{SCAP}}$ and $V_{\text{SCAP}} > 1.8\text{V}$** (e.g. if light level falls with the supercapacitor partially or fully charged)


CAP- Notes on the NFET Bypass Circuit

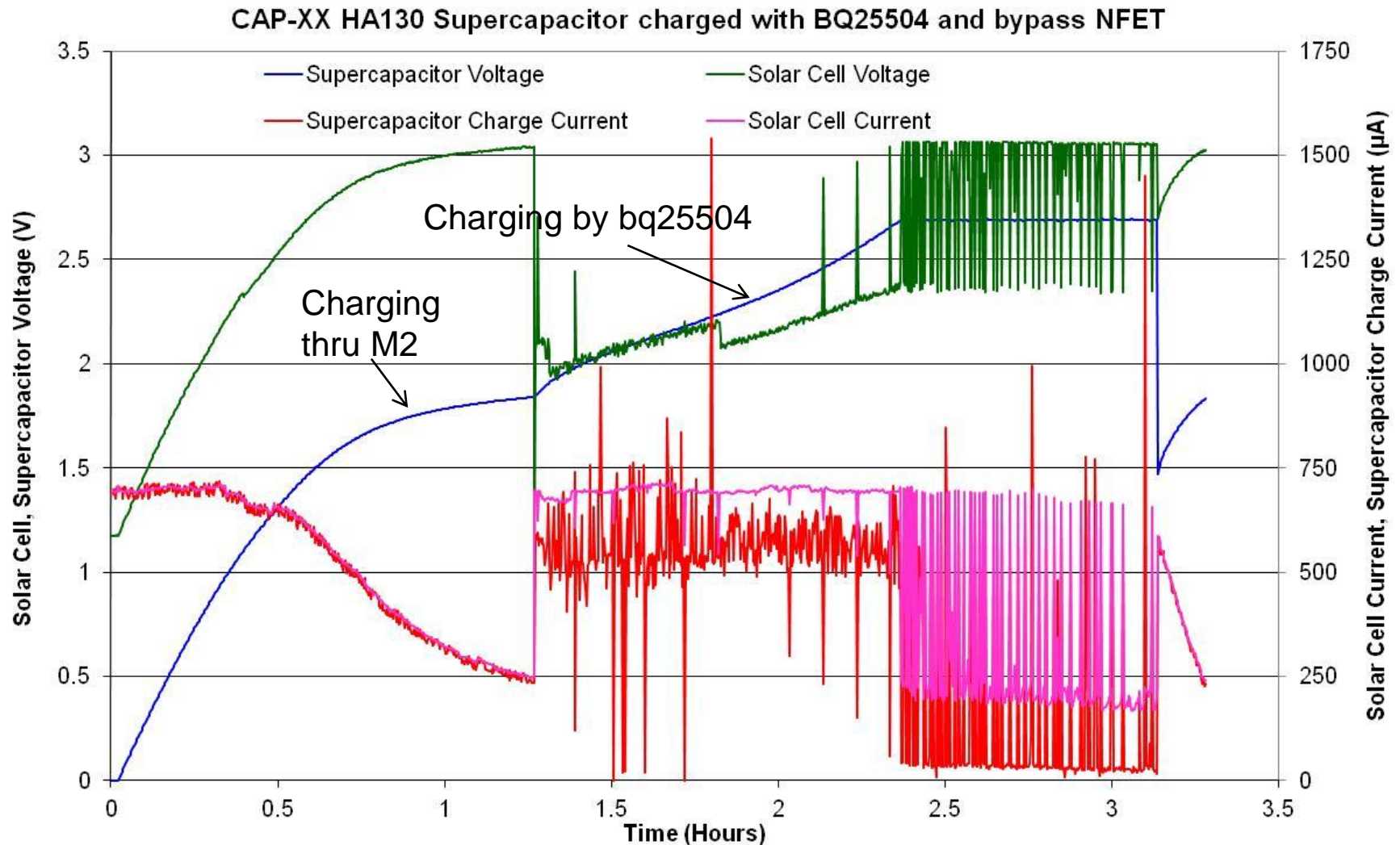1. When the unit first powers ON with the supercapacitor at 0V, the source of M2 is at 0V, U1 is OFF and R1 turns M1 OFF, preventing the bq25504 from operating
2. When $V_{\text{SOLAR}} > V_{\text{GSTH}}$ of M2, M2 starts to conduct, charging the supercapacitor
3. The resistance across M2 loads the solar cell so its voltage is just above $M2(V_{\text{GSTH}}) + V_{\text{SCAP}}$ so the solar cell provides good charge current in reasonable light
4. When $V_{\text{SCAP}} = 1.85\text{V}$, the o/p of U1 goes low, turning M2 OFF, and turning M1 ON. This enables the bq25504 when the voltage at $V_{\text{BAT}} > V_{\text{STOR_CHGEN}}$, so the IC always operates in PPT mode and never in cold start mode
5. Select a low power open drain comparator with in-built reference and which operates at a supply voltage down to 1.8V or less. In our example, we used a TLV3011, which has a typical quiescent current of $2.8\mu\text{A}$ and $V_{\text{REF}} = 1.242\text{V}$. An alternative is MAX9016 with a typical quiescent current of $1\mu\text{A}$ and $V_{\text{REF}} = 1.236\text{V}$
6. Select M2 with the lowest V_{GSTH} possible, with suitable size and gate charge. The lower the V_{GSTH} , the faster the supercapacitor will reach 1.85V and enable PPT mode in the bq25504. We have used an irlm6246, which has typical V_{GSTH} of 0.8V
7. The other components used in slide 9 were: M1 = FDV302P, R1 = $1\text{M}\Omega$, R2 = $10\text{M}\Omega$, R3 = $220\text{K}\Omega$, R4 = $680\text{K}\Omega$, R5 = $1.5\text{M}\Omega$.
8. The hysteresis in the circuit means U1 will go low when $V_{\text{BAT}} > 1.85\text{V}$ and U1 will go open drain when $V_{\text{BAT}} < 1.77\text{V}$







- Achieves a fast initial charge + fast charge with PPT once $V_{SCAP} > 1.8V$
- Diode prevents supercapacitor discharging into solar cell if light level falls
- Supercapacitor charged to 2.7V in 2hrs 25min, compared to 3hrs 30mins for direct charging
- HA130 provides excellent energy storage & power delivery in this architecture
- NFET bypass offers a fast charge solution AND will charge if $V_{SOLAR} < V_{SCAP}$ and $V_{SCAP} > 1.8V$ (e.g. if light level falls with the supercap partially or fully charged)
- There is a cost-performance trade-off between direct charging and PPT charging

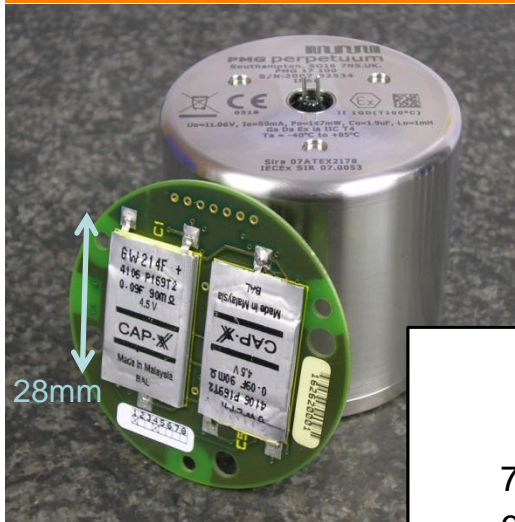


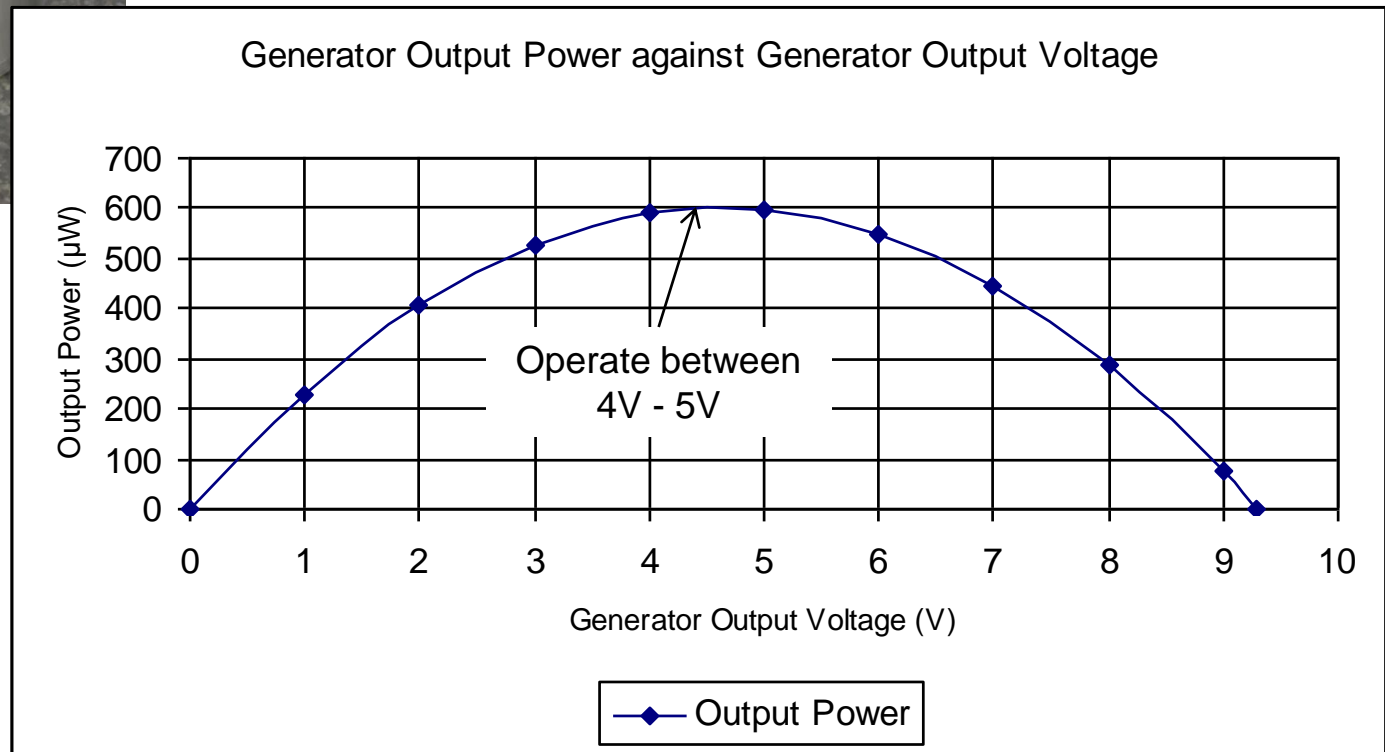- Perpetuum microgenerator is a high impedance source
- Power match circuit to keep PMG17 @ ~5V, supercap charge current regulated so PMG17 o/p voltage ~5V
- But what this data sheet curve doesn't tell you ...



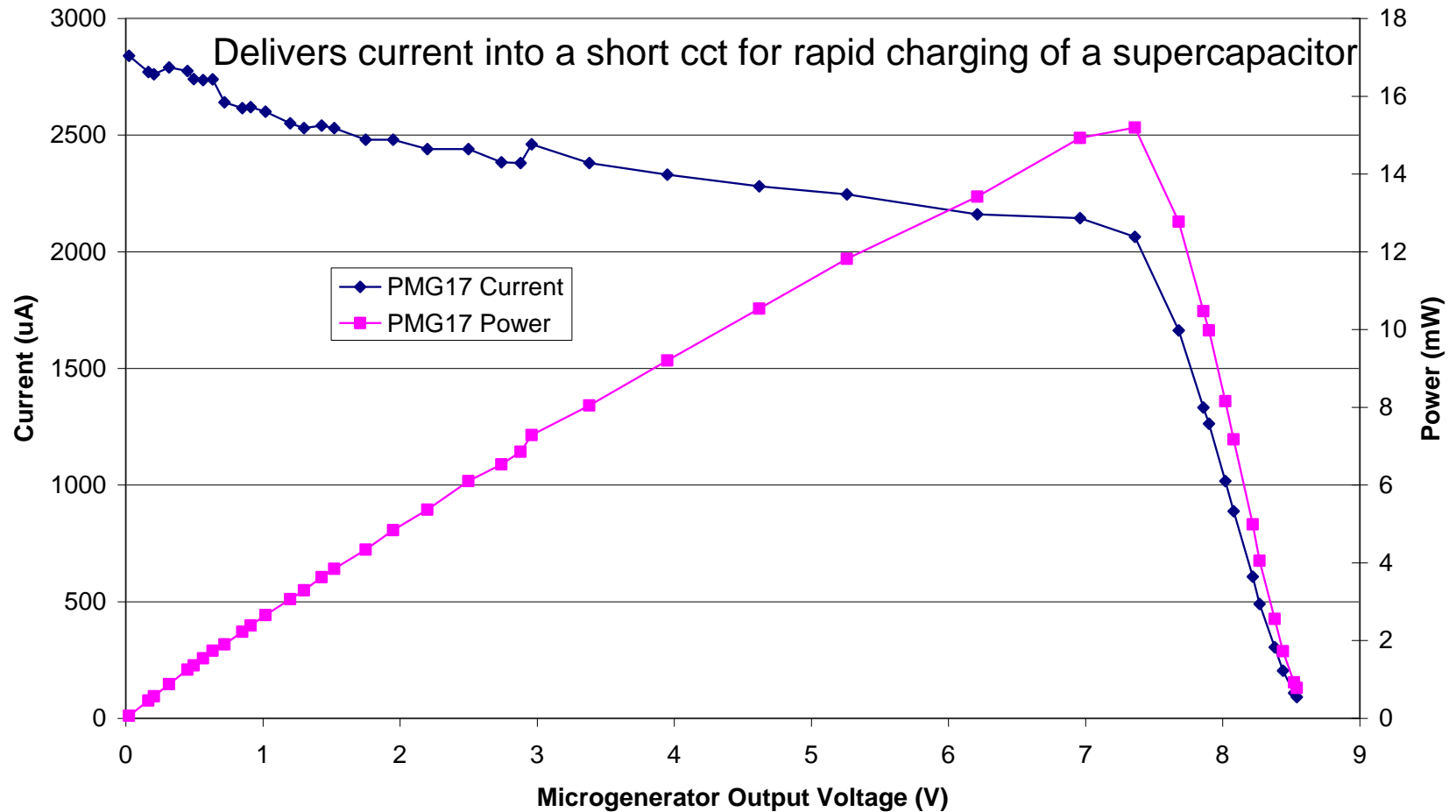Typical Micro Generator Output
Perpetuum PMG17



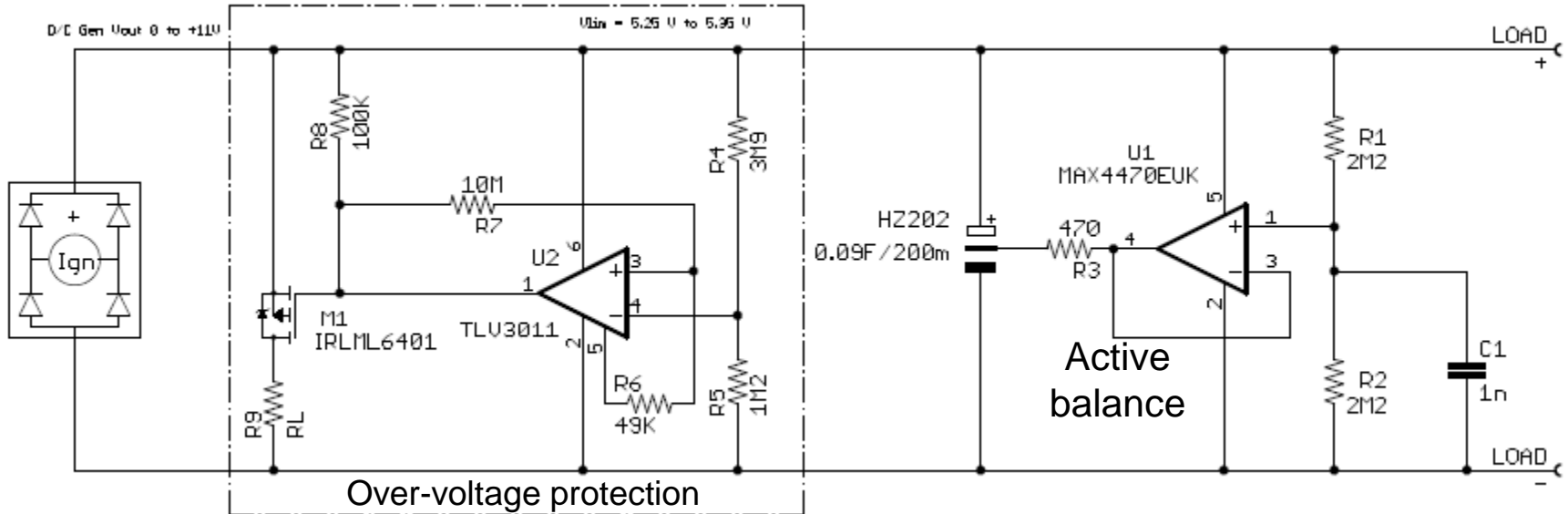


- U_2 is open drain. When $V_{OUT} < 1.8V$ (V_{SS_MIN}), U_1 o/p is open cct and R_8 keeps M_1 OFF
- Hysteresis on U_2 , turn M_1 ON when $V_{OUT} > 5.35V$, turn M_1 OFF when $V_{OUT} < 5.25V$
- Equivalent cct of microgenerator shows it is not possible for the supercap to discharge into it when its o/p voltage $< V_{SCAP}$, therefore do not need any reverse current protection
- Quiescent current of MAX4470 $\approx 1\mu A$, TLV3011 $\approx 3\mu A$
- Choose R_L to set rate of supercapacitor discharge and to ensure that $R_L \times I_{MICROGEN} < V_{MAX}$, typical value $\sim 1K\Omega$

Need a Buck with:


- PPT
- Max $V_{IN} \geq 10V$
- Max $P_{SUPPLY} \ll 15mW$

- The only IC we found with PPT was LT3652 ...
- ... but I_{BOOST} when switching = 20mA, so $P_{IN} \approx 200mW$

- May consider LTC3388-3 buck converter. No PPT, with I_{BOOST} when switching $\sim 150\mu A$, so $P_{IN} \approx 1.5mW$

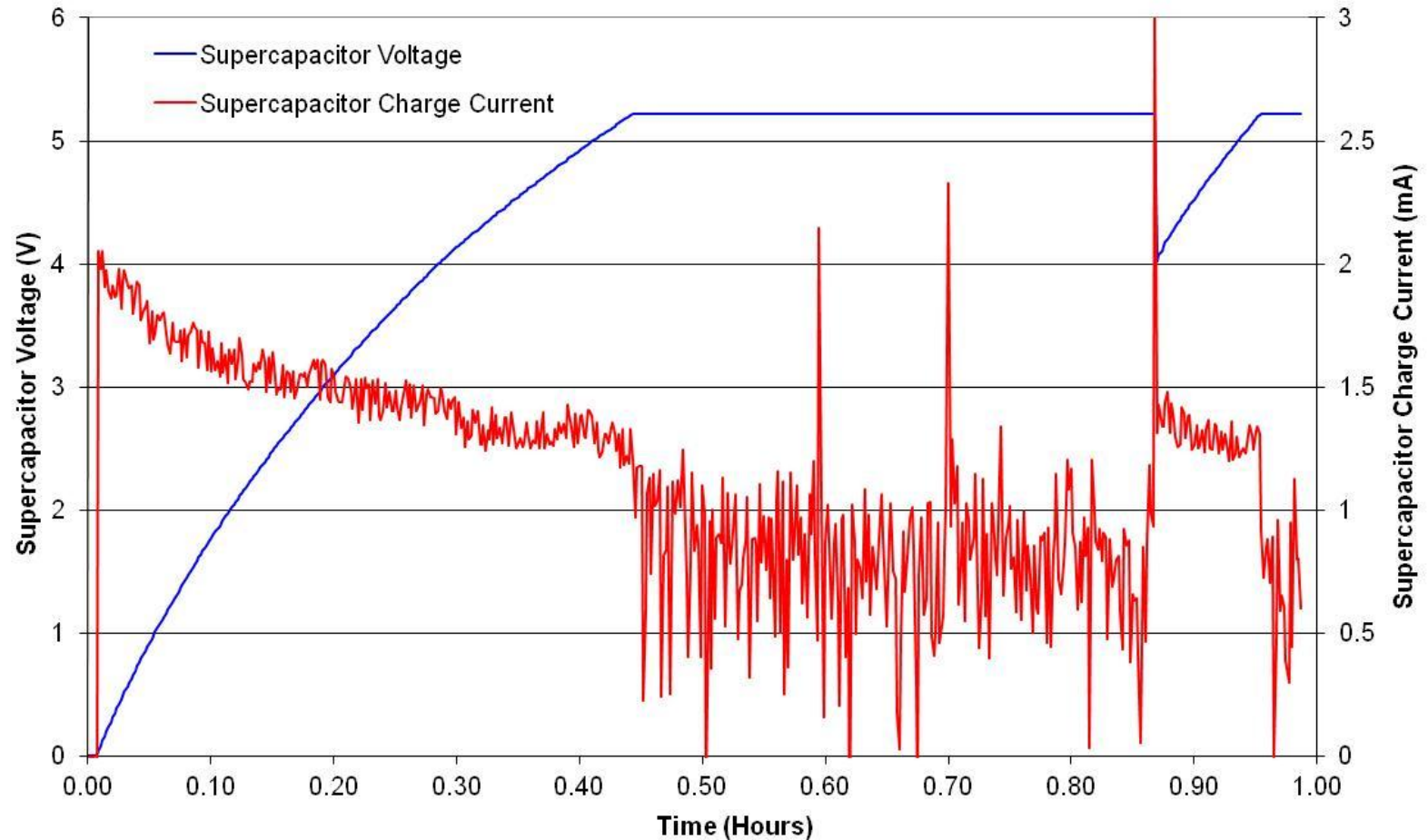CAP-XX HA230, 400mF, 140m Ω , 5.5V Supercapacitor charged to 5 Volts by Microgenerator

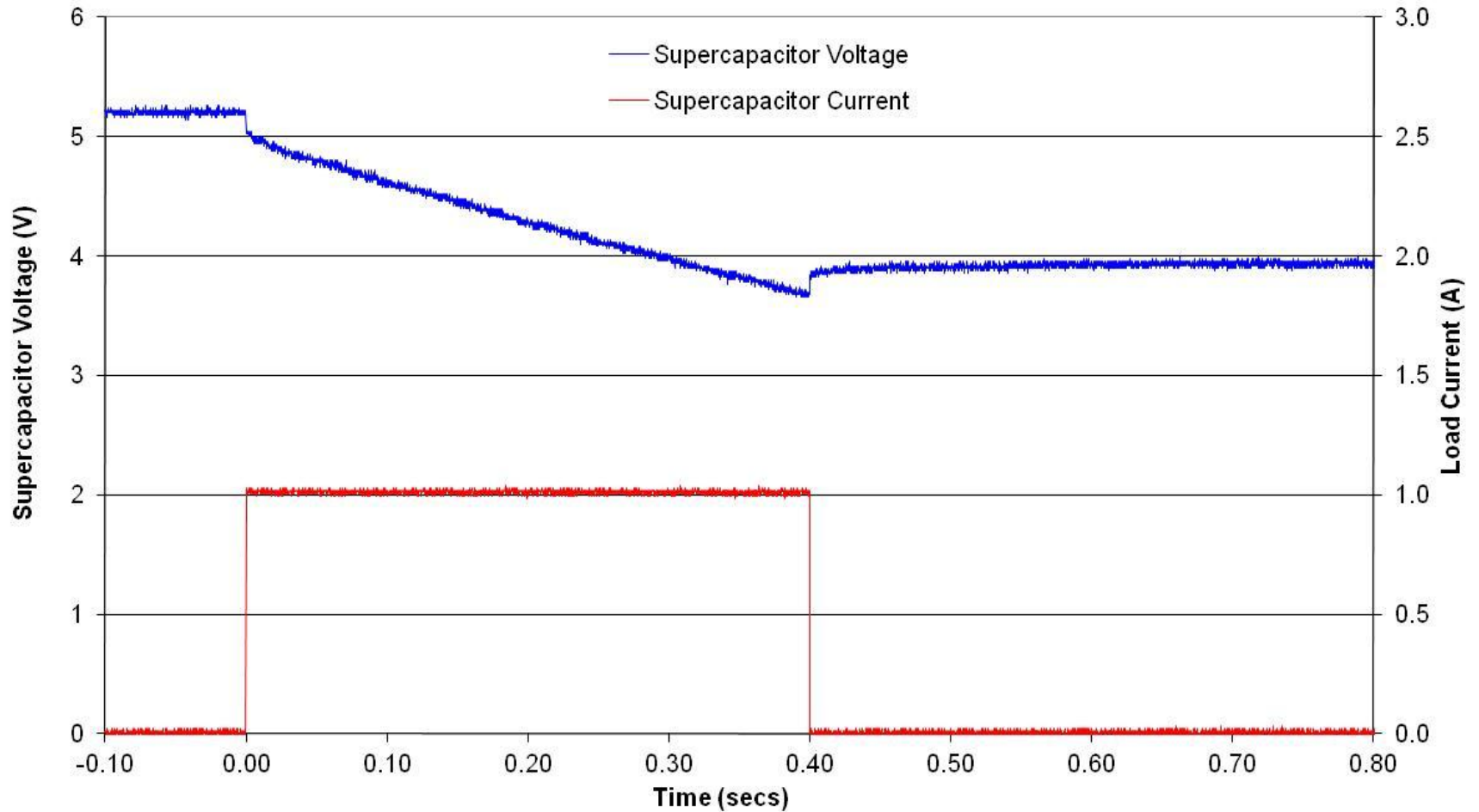Microgenerator Charged HA230 400mS Pulse Load



- PPT may reduce supercapacitor charging times, but probably by $< 50\%$ (depends on V-I characteristics of the energy harvester, V_{IN} and V_{OUT})
- Boost or buck-boost enables the supercapacitor to be charged even if the ambient energy falls so $V_{IN} < V_{OUT}$
- If V_{OUT} always $> V_{IN}$, direct charge may be best
- Need better PPT ICs that can charge into a supercapacitor and draw less current while switching
- A PPT IC which operated in switch mode as V_{OUT} increased from 0V to target voltage would be ideal
- There is a cost-performance trade-off between direct charging and PPT charging



CAP-XX

For more information, please contact

Pierre Mars

VP Quality & Applications Engineering

Email: pierre.mars@cap-xx.com

Web: www.cap-xx.com
