

- Supercapacitors as Power Buffers between Energy Harvesters and Wireless Sensors Pierre Mars
- Battery Power, September 18-19, 2012



The Problem

- Energy: The amount of work that can be done
- Power: The rate at which work is done (or at which energy is delivered)
- You can store energy, not power
- Energy harvesting sources have infinite energy but limited power
- Periodic wireless transmission requires bursts of energy at higher power than the energy harvester can deliver
- Supercapacitors buffer that power gap:
 - They are charged at low power from the harvester
 - And deliver bursts of energy at high power to the load



Agenda

- Why use a supercapacitor?
- Supercapacitor properties (What you need to know when designing your system)
 - What's inside
 - Power buffer
 - Temperature performance
 - Leakage current
 - Charge current
 - Cell Balancing
 - Ageing
- Supercpacitor circuits
- Interfacing the supercapacitor to your energy source



- Physical charge storage
 - → "Infinite" cycle life
- Low impedance (ESR)
 - → High power delivery
 - → Transmission over a cellular network
- High power delivery at low temps (-40°C)
- Easy to charge
 - → Just need a charge current & over-voltage protection
- Low leakage current
- Available in thin, small form-factors





What's Inside?

A supercapacitor is an energy storage device which utilizes high surface area carbon to deliver much higher energy density than conventional capacitors



CAP- Supercapacitor as a Power Buffer

- Average load power < Average source power
- System design with:
 - Interval between peaks, Peak power, Energy source, Harvester size, Efficiency
 High Peak Power



- Source sees constant power load (set at maximum power point?)
- Load sees low impedance source that delivers high peak power for the required duration
 - Low ESR = high power; High C = delivered for required duration



Excellent Performance across a Wide Temperature Range



Normalised ESR vs Temp



Poor Frequency Response ...





...but Excellent Pulse Response

Case 2 - Nokia BL6C Battery + CAP-XX Supercapacitor





$C_{\text{EFFECTIVE}}$ as a Function of PW







Ceff Observed vs SPICE simulation, CAP-XX GS203





Supercapacitor Leakage Current

Leakage Current





Supercapacitors Need a Minimum Initial Charging Current ...

Charging at 20uA





...but a Short Initial Charge at "High" Current can Overcome this

HZ102 charging to 2.5V at 5uA after varying time at pre-charge at 2.5V, 10mA





Cell Balancing is Required

Leakage Current





Simple Passive Balancing



- The purpose of this circuit is to maintain V_M close to V_{SCAP} / 2
- $V_M = R_B x I_{BR2} = R_B x (I_{BR1} Balancing Current)$
- For this circuit to work, Balancing Current must be << I_{BR1}, I_{BR2}
- VM must be prevented from going >> V_{SCAP} / 2 or << V_{SCAP} / 2 for any significant length of time
- SIMPLE but HIGH CURRENT SOLUTION (~100µA through the resistors)

Active Balance Circuit for Very Low Leakage Current

 2 capacitor cells in series need voltage balancing, or slight differences in leakage current may result in one cell going overvoltage

CAP-

- Low current rail-rail op amp, < 1μA
- Can source or sink current, 11mA
- Supplies or sinks the difference in leakage current between the 2 cells to maintain balance











- Supercapacitors use physical not electrochemical charge storage
- Ageing is a function of time at temperature and voltage, not number of cycles
- Determine expected ageing from operating profiles (voltage and temp combinations) and their duty cycle
- Size the supercapacitor so you have the required C & ESR at end of life after allowing for ageing



Supercapacitor Ageing: C Loss





GW214 ESR @ 3.6V, 23C, Ambient RH





Supercapacitor Interface Circuits

Design principles:

- 1. Must behave gracefully into a short circuit
- 2. Must start charging from 0V
- 3. Must provide over-voltage protection
- 4. Must prevent the supercapacitor from discharging into the source
- 5. Should be designed for maximum efficiency



- A discharged supercapacitor will look like a short circuit to your energy source
- Most energy harvesters don't care will deliver current into a short circuit
- Definitely a problem for batteries, and some other power supplies
 - Interface electronics must manage this either in the design:
 - Keep the source near its maximum power point
 - Graceful behaviour into a short circuit
 - Or with a separate current limit
 - AAT4610 (www.cap-xx.com/resources/app_notes/an1002.pdf
 - Or with a supercapacitor charging IC
 - LTC3225



Example 1: Solar cells



Simplified Circuit Model of a Solar Cell

XOB17, 22mm x 7mm x 1.6mm used for measurements in following slides



- ${\rm I}_{\rm PH}$ generates current α light falling on the cell
- If no load connected all the current flows through the diode whose forward voltage = V_{OC}.
- RP represents leakage current
- RS represents connection losses, usually not significant

- Will deliver current into a short circuit (discharged supercapacitor)
- Will discharge the load if light level drops



Simple to Characterise your Solar Cell in your Conditions

Cell Current/Voltage Behavior





Direct Charging Circuit



- Simplest circuit, starts charging from 0V
- V_{oc} < 2.7V at maximum light level
- D1 prevents the supercapacitor from discharging back into the solar cell when light levels fall
- BAT54 chosen for D1 due to low V_F . V_F is <0.1V at currents < 10µA
- HA130 provides excellent energy storage & power delivery
- Fastest charge. But will NOT charge if V_{SOLAR} < V_{SCAP} (e.g. if light level falls)



Fast Charging Waveforms

HA130 Direct Charge



© CAP-XX 2012 27



Pulse Current Discharge from the Supercapacitor

Direct Solar Charged HA130 on 1 Amp 800mS Discharge





Example1: Microgenerators



- Perpetuum microgenerator is a high impedance source
- Power match circuit to keep PMG17 @ ~5V, supercap charge current regulated so PMG17 o/p voltage ~5V
- But what this data sheet curve doesn't tell you ...

Generator Output Power against Generator Output Voltage





Microgenerators: Characterise the Device for yourself ...

Typical Micro Generator Output Perpetuum PMG17





Charging cct: Microgenerator with 800mF Supercapacitor



- Shunt regulator provides over voltage protection, set to 5V, with small (~20mV) hysteresis so little energy dissipated from supercapacitor.
- Active balance cct maintains cell voltages
- Diode bridge around microgenerator prevents supercapacitor from discharging back into the coil



CAP-XX HA230, 400mF, 140mΩ, 5.5V Supercapacitor charged to 5 Volts by Microgenerator





Pulse Current Discharge from The Supercapacitor

Microgenerator Charged HA230 400mS Pulse Load





Peak Power Tracking

$I_{OUT} = P_{IN}.\eta / V_{OUT}$

Maximise I_{OUT} if P_{IN} = Peak Power of energy source

Not many low power PPT Ics

Some have fixed o/p voltage (assume Li-Ion battery), or do not behave gracefully into a supercapacitor at 0V (assume a short cct on a battery and inhibit charging)

Example: Using bq25504 charging an 800mF supercapacitor from a solar cell providing ~1.5mW





Discharged battery will be ~70% of charge V, but discharged supercapacitor is at 0V

> For both Buck & Boost, when $V_{OUT} << V_{IN}$, the Control turns Q1 ON (with current sense/limit), & Q2 OFF, until $V_{OUT} >$ predetermined threshold. Reduces to direct charging





Charge with bq25504 with NFET Bypass for Rapid Charge from 0V



- Supercap charges directly from 0V using NFET M2 to bypass bq25504. M1 is OFF, stopping the bq25504 from pulling down the solar cell voltage
- When the supercap reaches ~1.8V, the comparator turns M1 ON, connecting the bq25504 to the solar cell, and turns M2 OFF, preventing the solar cell overcharging the supercap if V_{SOLAR_OC} > V_{SCAP_MAX}
- The supercapacitor target voltage is now set by the bq25504. There is no possibility of the supercapacitor being over-voltage
- Achieve fast initial charge + fast charge with PPT once V_{SCAP} > 1.8V
- Fast charge, and WILL charge if V_{SOLAR} < V_{SCAP} and V_{SCAP} > 1.8V (e.g. if light level falls with the supercapacitor partially or fully charged)



Waveforms for Charging with bq25504 and NFET Bypass





Peak Power Tracking

- + $I_{OUT} = P_{IN}.\eta / V_{OUT}$
 - Maximise I_{OUT} if P_{IN} = Peak Power of energy source

But supercapacitors are not charged at constant V, so some questions:

- Quiescent current?
 - Will it work?
 - I_Q of IT3652, buck with PPT (20mA) cf Power of μgen (~2mA)
- Behaviour into a supercapacitor at 0V (short cct)
- Behaviour when $V_{OUT} \ll V_{IN}$
- + Boost, Buck-Boost
 - Will charge supercap if V_{ENERGY_SOURCE} < V_{SCAP}
- Is it simpler/cheaper to make the open cct V of the energy harvester
 >= supercap max V?
- ? Is the energy harvester average power sufficient without PPT?



- Ideal power buffer
- Low voltage cells -> multiple cells -> cell balancing
- Leakage current decays over time. Charging may take longer than expected
- Allow for ageing when selecting initial C & ESR
- Solar cells and Microgenerators will deliver max current into a short circuit (ideal for charging a supercapacitor from 0V)
- Need to prevent the supercapacitor discharging back into the solar cell when light level falls
- O/C voltage of energy harvesting source. Is it cheaper to increase this and use direct charging?



CAP-X

For more information, please contact Pierre Mars VP Quality & Applications Engineering Email: <u>pierre.mars@cap-xx.com</u>

Web: www.cap-xx.com